


Name : Ibrahim Isaa

Matric : M&amp;E131137


Question : For <sup>the</sup> push-pull CS amp

(a) determine the zero for the gain equation

(b) determine the equation for the pole.

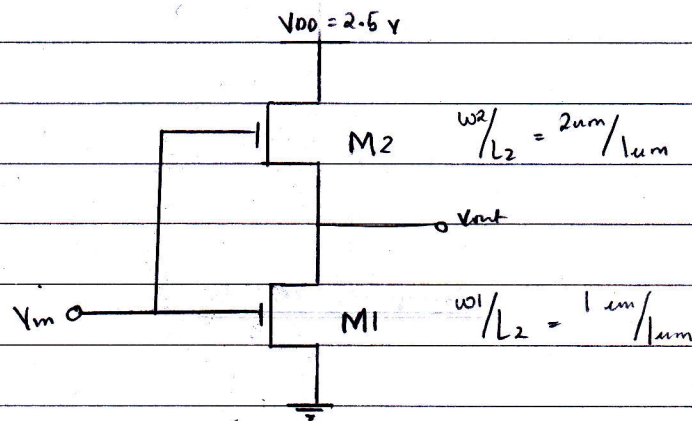

Solution :


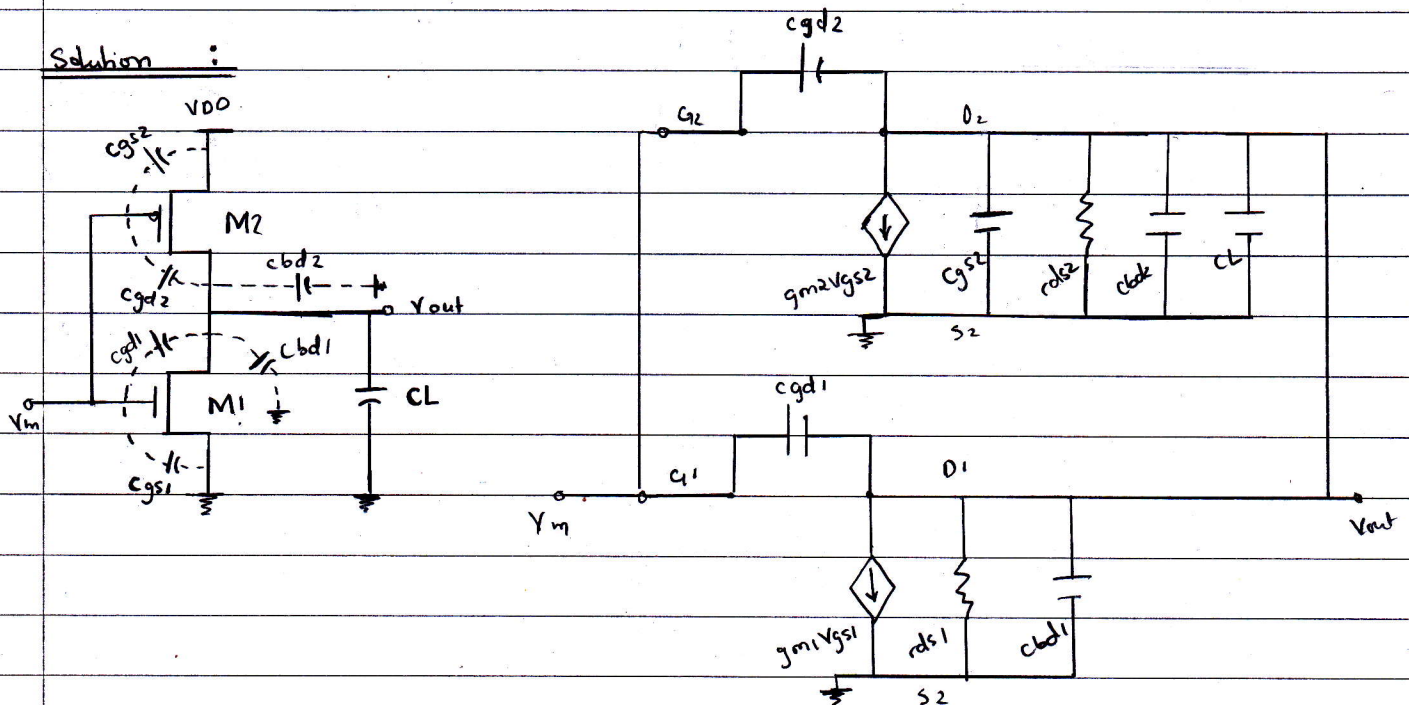


Small Signal Equivalent  
Circuit



Subject :

Date:

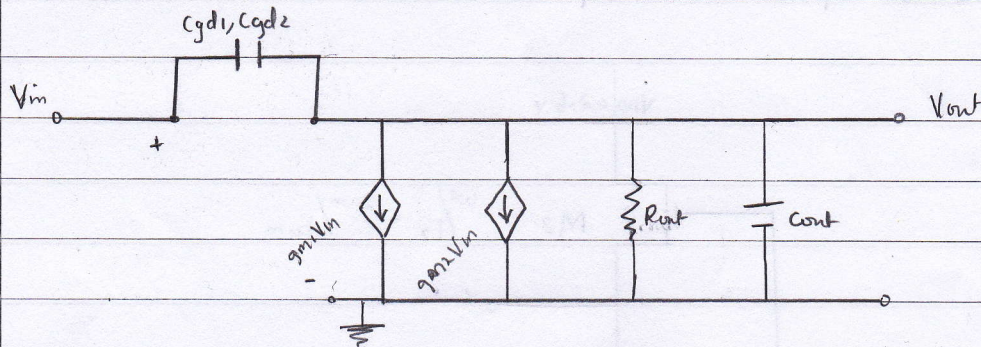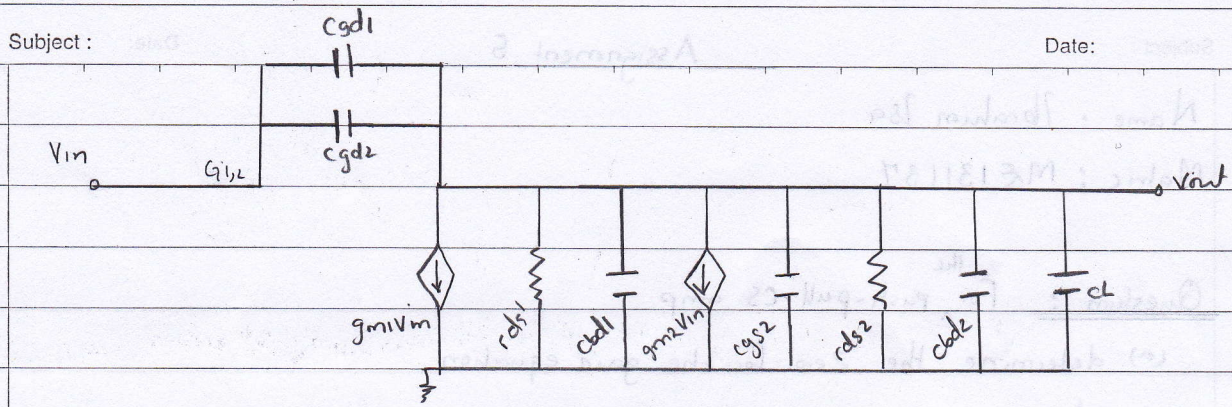Simplified circuit

$$R_{out} = r_{ds1} \parallel r_{ds2} ; C_{out} = C_{bd1} + C_{gs2} + C_{bd2} + C_L$$

Gain ( $A_v$ ) :

$$s(C_{gd1} + C_{gd2})(V_{out} - V_m) + g_{m1}V_m + g_{m2}V_m + V_{out}/R_{out} + sC_{out}V_{out} = 0$$

$$s(C_{gd1} + C_{gd2})V_{out} + V_{out}(1/R_{out} + sC_{out}) = s(C_{gd1} + C_{gd2})V_m - V_m(g_{m1} + g_{m2})$$

$$\therefore \frac{V_{out}}{V_m} = \frac{s(C_{gd1} + C_{gd2}) - (g_{m1} + g_{m2})}{s(C_{gd1} + C_{gd2}) + (1/R_{out} + sC_{out})}$$

$$= \frac{-(g_{m1} + g_{m2})}{1/R_{out}} \times \frac{\left(1 - \frac{s(C_{gd1} + C_{gd2})}{(g_{m1} + g_{m2})}\right)}{\left(1 + \frac{s(C_{gd1} + C_{gd2} + C_{out})}{1/R_{out}}\right)}$$

$$\therefore A_v = \frac{V_{out}}{V_m} = -R_{out}(g_{m1} + g_{m2}) \left[ \frac{1 - s(C_{gd1} + C_{gd2})/(g_{m1} + g_{m2})}{1 + sR_{out}(C_{gd1} + C_{gd2} + C_{out})} \right]$$



Subject :

Date:

Poles : Value of  $s$  when the denominator is "0"

$$1 + sR_{out}(C_{gd1} + C_{gd2} + C_{out}) = 0$$

$$sR_{out}(C_{gd1} + C_{gd2} + C_{out}) = -1$$

$$\therefore s = - \frac{1}{R_{out}(C_{gd1} + C_{gd2} + C_{out})}$$

$$R_{out}(C_{gd1} + C_{gd2} + C_{out})$$

~

Zero : Value of  $s$  when the numerator is "0"

$$1 - \frac{s(C_{gd1} + C_{gd2})}{g_{m1} + g_{m2}} = 0$$

$$g_{m1} + g_{m2}$$

$$+ \frac{s(C_{gd1} + C_{gd2})}{g_{m1} + g_{m2}} = +1$$

$$g_{m1} + g_{m2}$$

$$\therefore s = \frac{g_{m1} + g_{m2}}{(C_{gd1} + C_{gd2})}$$

$$(C_{gd1} + C_{gd2})$$

~